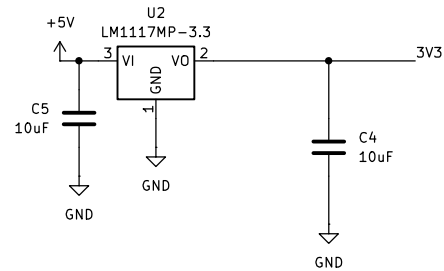


LDO 3V3 regulator

You might be wondering why is there an external regulator?


Well, the arduino 3V3 power output does not provide enough current to ensure LNA functionality, so we need to implement this Low dropout regulator

The coupling capacitors have been implemented following the LDO's datasheet




nRF24 with PA+LNA module

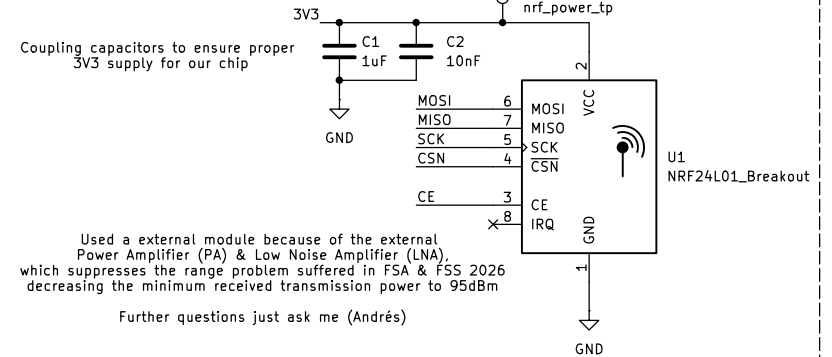
Placed to be able to test correct supply to the module



Arduino Nano 3.0 with USB-C connector

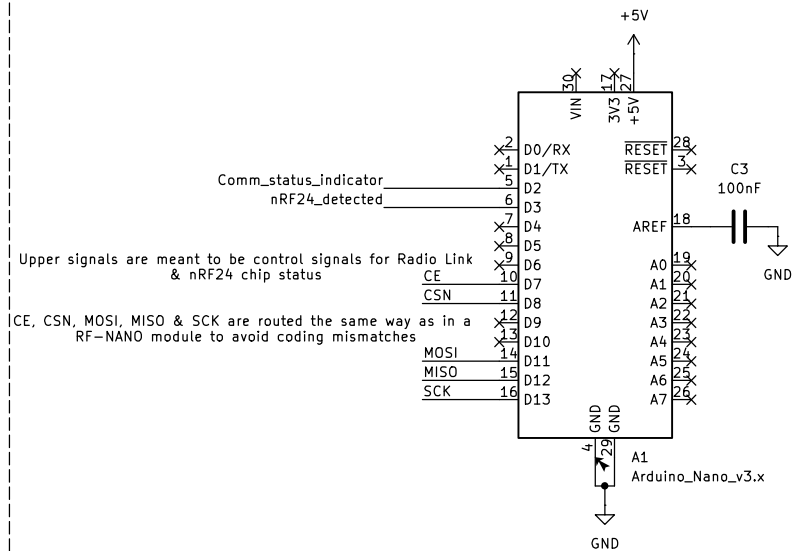

LED indicators for radio status

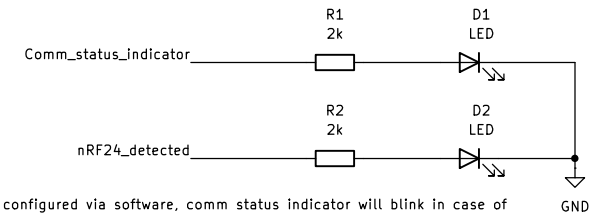

It will be configured via software, comm status indicator will blink in case of active transmission or on if radio link is established.

nRF24 detected will be on when the radio chip is detected by the arduino, to isolate problems related to the nRF24L01 breakout module